


WALKING BOT

By Lucas

May 2025

Development Pipeline

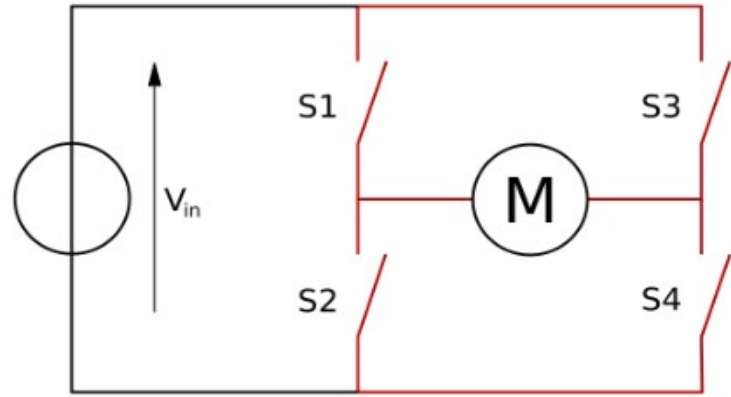- Create code for device
- Compile (change code into 0s and 1s)
- Upload (put the compiled code onto device)
- Have fun!



H-bridge

An H-bridge is how a motor works. If S1 and S4 are turned on, then the motor will spin one way. If S2 and S3 are turned on, then the motor will spin the other way.

If S1/S2 or S3/S4 are turned on at the same time then the battery will do at least one of these three things:

- Heat up
- Blow up
- Burn your house down


This is because that connecting the positive and negative of a battery together causes the electricity to go extremely fast between the terminals. When the electricity goes through the motor, the motor creates resistance for the electricity as the electricity has to make the motor spin before it can go back to the other battery terminal.

What is a PWM?

A PWM (Pulse Width Modulation) is something that converts digital (on and off) power to analog (any amount of power). It is in every single type of electronic device that has some kind of processor, as it is used for computing things.

For example, if you wanted to get half the power from a 1(max power) a computer would have to use a PWM so that it could find it out. It would do this by saying that 1 was 100 analog power then it sent analog 50 power. This is what H-bridges are used for.

Schematic

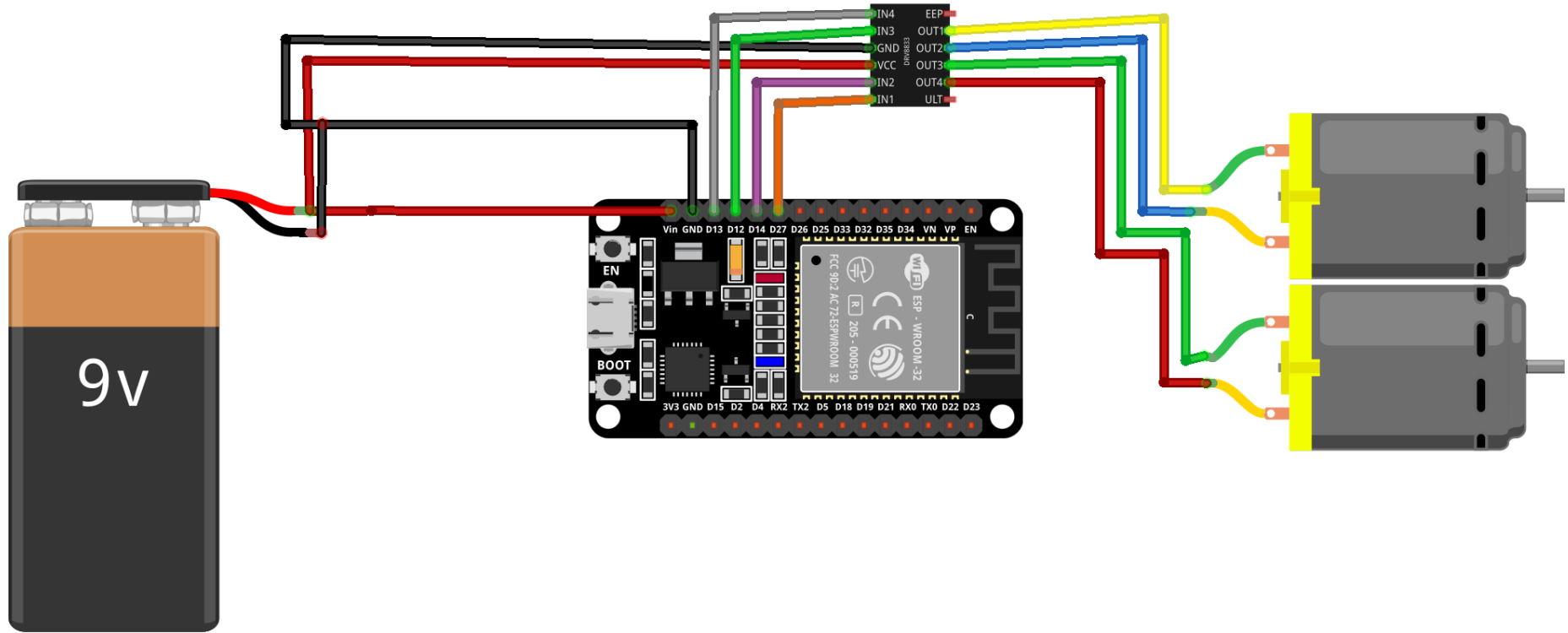

What is a PWM?

A PWM (Pulse Width Modulation) is something that converts digital (on and off) power to analog (any amount of power). It is in every single type of electronic device that has some kind of processor, as it is used for computing things.

For example, if you wanted to get half the power from a 1(max power) a computer would have to use a PWM so that it could find it out. It would do this by saying that 1 was 100 analog power then it sent analog 50 power. This is what H-bridges are used for.

How to use

- Switch on from battery (or plug in USB wire)
- Connect to WiFi network “LucasPotato” with password “mypotato”
- If the captive portal does not appear, go to <http://192.168.4.1> in your web browser
- Set WiFi credentials
- Press Submit
- Restart the ESP32
- Connect to set WiFi network in Captive Portal
- Visit <http://esp32.local> in web browser
- Wait until it says “Ready” in top right corner
- Use it!

My very bad 3-D model

